

TRAFFIC LIGHT CONTROLLER PROJECT

1. Introduction

Traffic signals are an essential part of road management systems. This project focuses on the **Verilog implementation** of a **Traffic Light Controller** that operates at a **junction** using a **finite state machine (FSM)** approach. The design ensures that only one direction receives a green signal at a time, while others remain red, closely mirroring real-world traffic systems.

2. Problem Statement

The goal of this project is to design a **realistic traffic light controller** that follows the correct sequence of Red, Yellow, and Green signals for each direction, ensuring smooth traffic flow and safety. The system follows a well-defined **FSM-based operation** to control the lights and manage road intersections effectively.

4. Verilog Code Implementation

4.1 Traffic Light Controller (Design Code)

```
module Traffic_Light_Controller(  
    input clk, reset,  
    output reg [1:0] ns_light, // North-South Traffic Light (00 = Red, 01 = Yellow, 10 = Green)  
    output reg [1:0] ew_light, // East-West Traffic Light (00 = Red, 01 = Yellow, 10 = Green)  
    output reg ns_left, ew_left // Left Turn Allowed (1 = Yes, 0 = No)  
);  
  
    // Define State Encoding (Verilog-2005 compatible)  
    parameter S0 = 3'b000, // North-South Green  
             S1 = 3'b001, // North-South Yellow  
             S2 = 3'b010, // All Stop  
             S3 = 3'b011, // East-West Green  
             S4 = 3'b100, // East-West Yellow  
             S5 = 3'b101; // All Stop
```

```

reg [2:0] current_state, next_state;

reg [3:0] counter; // Timing Counter

// State Transition Logic

always @(posedge clk or posedge reset) begin

    if (reset)

        current_state <= S0;

    else if (counter == 10) // Change state every 10 clock cycles

        current_state <= next_state;

end

// Next State Logic

always @(*) begin

    case (current_state)

        S0: next_state = S1; // NS Green → Yellow

        S1: next_state = S2; // NS Yellow → All Stop

        S2: next_state = S3; // All Stop → EW Green

        S3: next_state = S4; // EW Green → Yellow

        S4: next_state = S5; // EW Yellow → All Stop

        S5: next_state = S0; // All Stop → NS Green

        default: next_state = S0;

    endcase

end

// Output Logic for Traffic Lights

always @(current_state) begin

    case (current_state)

        S0: begin // North-South Green, East-West Red

```

```
    ns_light = 2'b10; ew_light = 2'b00;

    ns_left = 1; ew_left = 0;

end

S1: begin // North-South Yellow, East-West Red

    ns_light = 2'b01; ew_light = 2'b00;

    ns_left = 1; ew_left = 0;

end

S2: begin // All Stop (Red)

    ns_light = 2'b00; ew_light = 2'b00;

    ns_left = 0; ew_left = 0;

end

S3: begin // North-South Red, East-West Green

    ns_light = 2'b00; ew_light = 2'b10;

    ns_left = 0; ew_left = 1;

end

S4: begin // North-South Red, East-West Yellow

    ns_light = 2'b00; ew_light = 2'b01;

    ns_left = 0; ew_left = 1;

end

S5: begin // All Stop (Red)

    ns_light = 2'b00; ew_light = 2'b00;

    ns_left = 0; ew_left = 0;

end

default: begin

    ns_light = 2'b00; ew_light = 2'b00;
```

```
        ns_left = 0; ew_left = 0;
    end
endcase
end

// Counter for Timing
always @(posedge clk) begin
    if (counter == 10)
        counter <= 0;
    else
        counter <= counter + 1;
    end
endmodule
```

4.2 Testbench Code

```
module testbench;

    reg clk, reset;

    wire [1:0] ns_light, ew_light;
    wire ns_left, ew_left;

    // Instantiate the Traffic Light Controller
    Traffic_Light_Controller uut (
        .clk(clk),
        .reset(reset),
        .ns_light(ns_light),
        .ew_light(ew_light),
        .ns_left(ns_left),
```

```
.ew_left(ew_left)

);

always #5 clk = ~clk; // Toggle every 5 time units

initial begin

    // Initialize Signals

    clk = 0;

    reset = 1;

    #10 reset = 0; // Release Reset

    // Run Simulation for 100 time units


    #100 $stop;

end


endmodule
```

5. Simulation Results & RTL Schematic

5.1 Finite State Machine (FSM) Diagram:

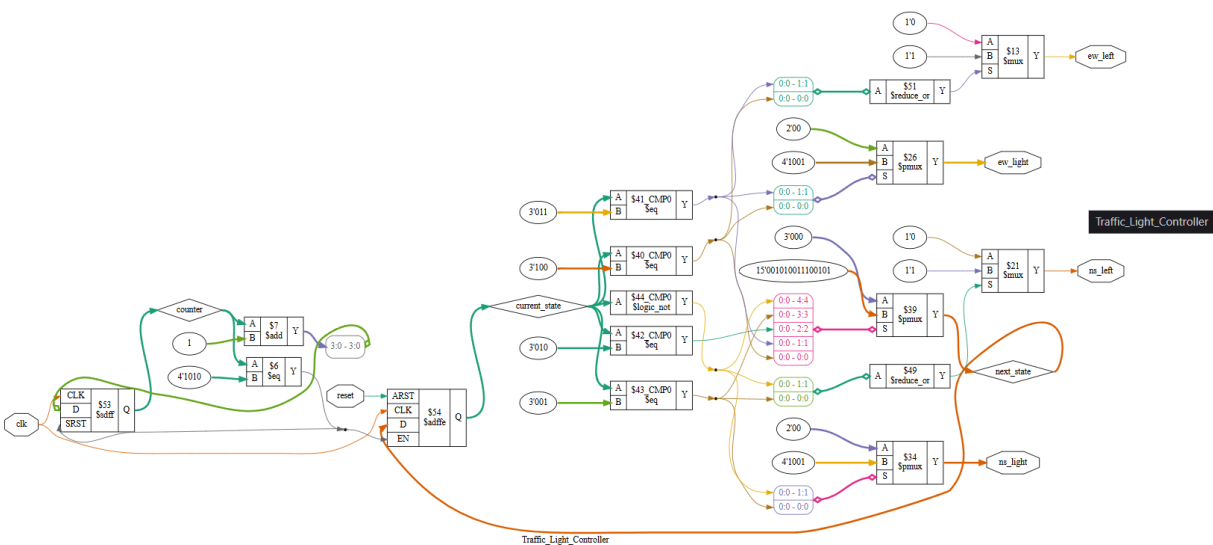


5.2 RTL Schematic

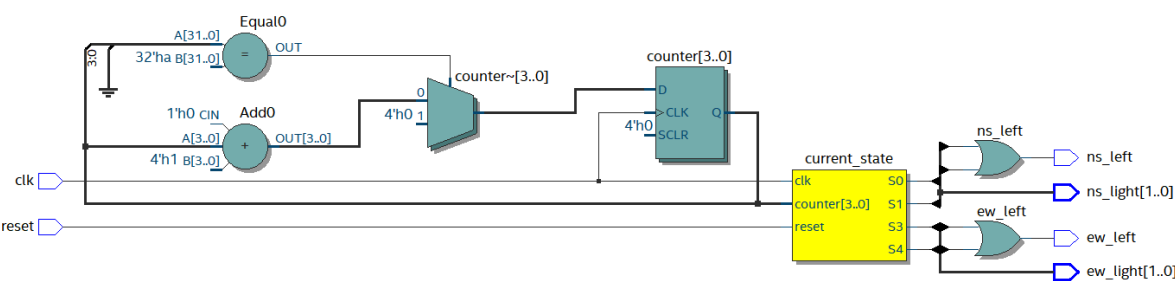


5.3 FPGA Gate Level Implementation


Post-Mapping:

 

Post-Fitting:

 


5.4: Output Waveform:

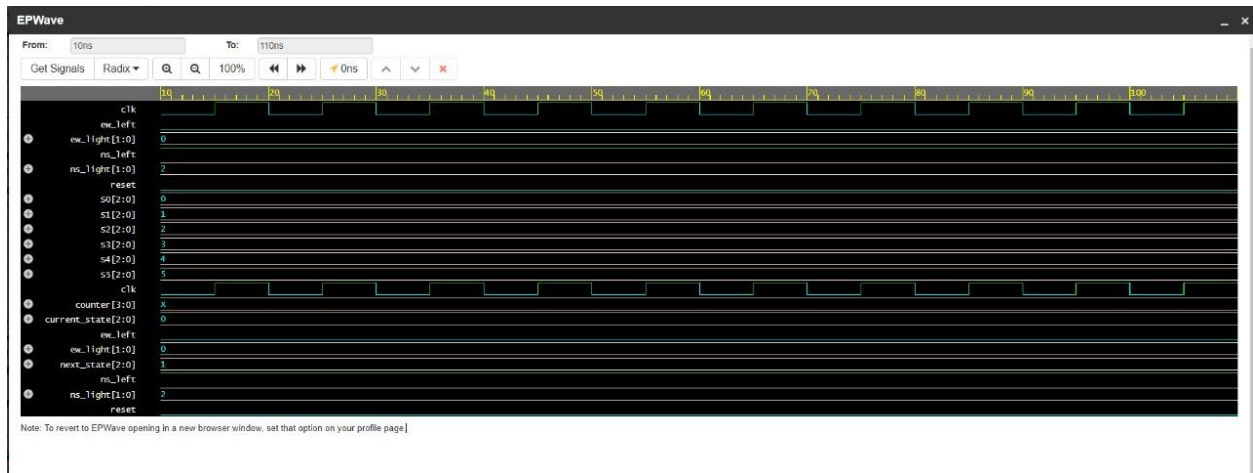

6. Reports After Synthesis

- Timing Report

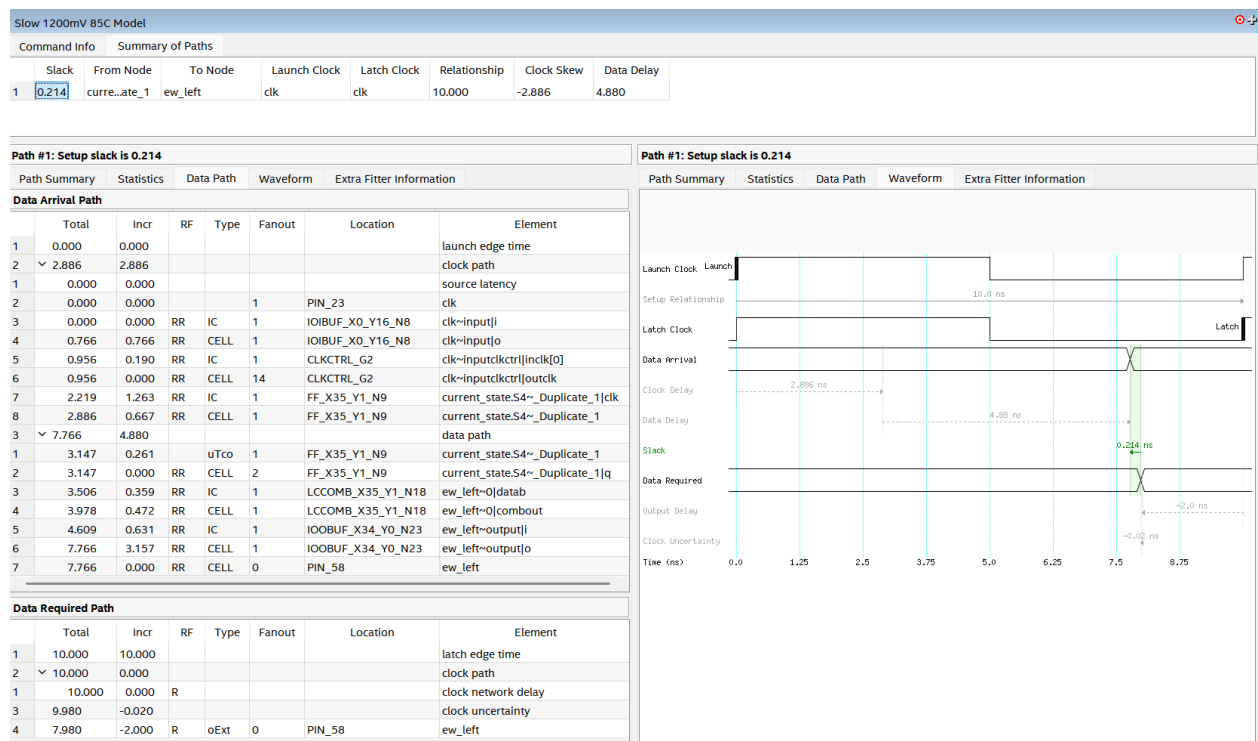

7. Conclusion

The designed Traffic Light Controller successfully simulates the FSM-based traffic system. The simulation results confirm that the system transitions correctly between states, ensuring smooth and safe traffic management.

8. References

1. FPGA-based Digital Design References
2. NPTEL Lectures on Digital Design
3. ASIC-World Verilog FSM Guide
4. Cyclone IV E EP4CE22E22C8 Pinouts